

OGUN DIGICLASS

**CLASS: SECONDARY
SCHOOL**

SUBJECT: PHYSICS


TOPIC: SIMPLE

ALTERNATING CURRENT



www.ogundigiclass.ng

CIRCUITS



Alternating current

The diagram illustrates the generation of alternating current. A black power plant with a cooling tower is shown with a wavy yellow line representing AC power being transmitted. In the background, there is a blue grid representing a city and a blue square with a white '1' and a black square with a white '2'. A circular icon with a question mark is also present.



Direct current


The diagram illustrates the generation of direct current. A battery with a blue lightning bolt symbol is shown with a straight yellow line representing DC power being transmitted to a smartphone. In the background, there are various electronic components like a capacitor and a resistor.

SIMPLE ALTERNATING
CURRENT CIRCUITS

Learning Objectives

- Explain the peak and R.M.S values of current and P.D
- Establish the phase relationship between current and P.D in an A.C. Circuit
- Explain reactance and impedance
- Determine current in circuits containing: resistance and inductance; resistance and capacitance; resistance, inductance and capacitance.
- Determine power in an A.C circuit


INTRODUCTION



An alternating current (A.C) is the current that varies sinusoidally in such a way as to reverse its direction periodically i.e current flow in the positive and negative direction periodically.




OFF

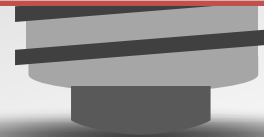


ON

INTRODUCTION

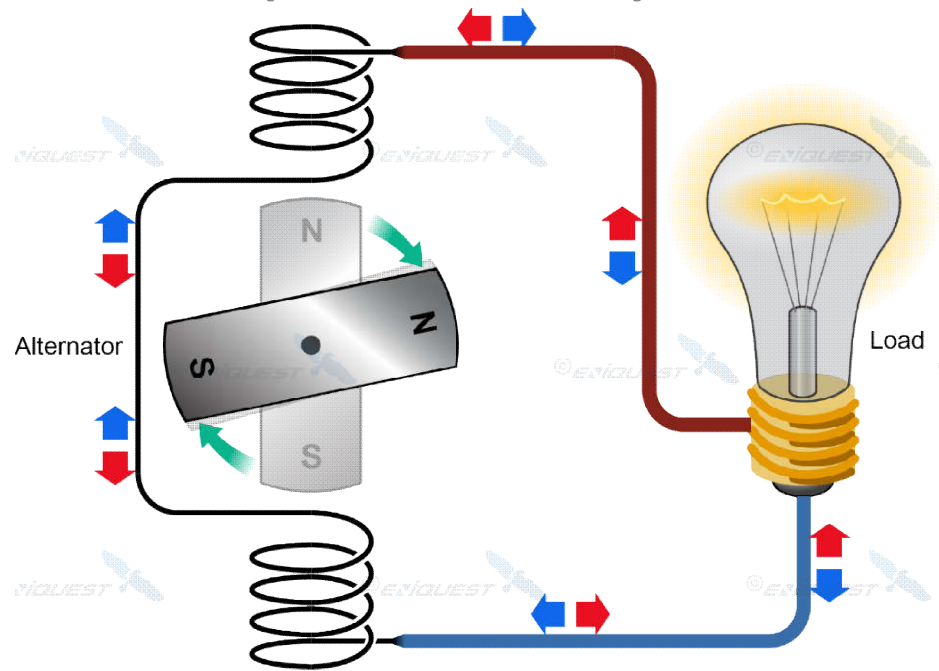An alternating current (A.C) is the current that varies sinusoidally in such a way as to reverse its direction periodically i.e current flow in the positive and negative direction periodically.



You may have noticed the letters a.c. on the power pack. This is **alternating current**. The electrons rapidly change direction. Alternating current can be provided by generators. Mains electricity is an alternating current.

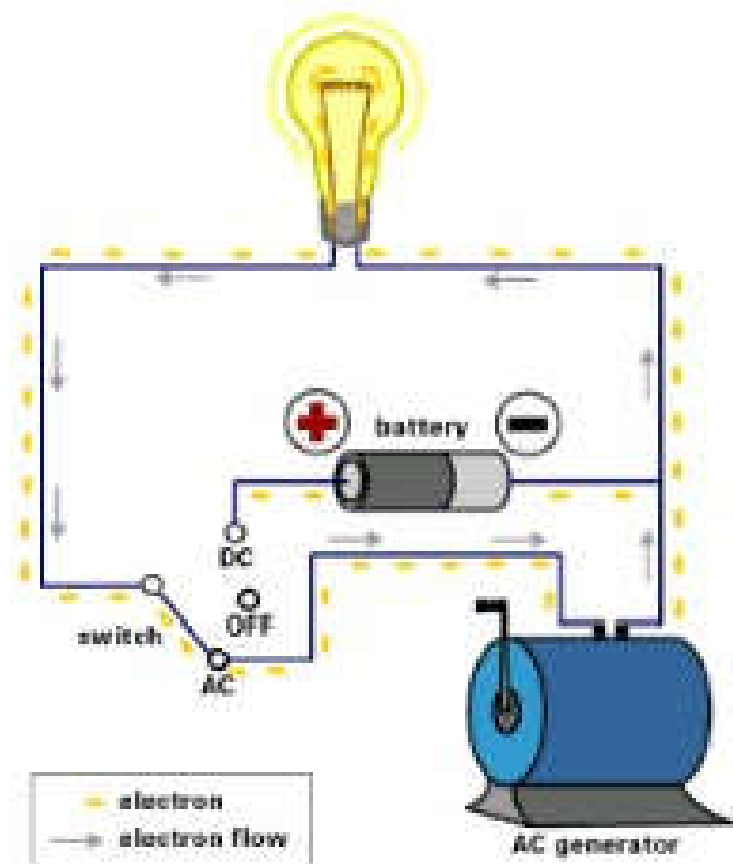

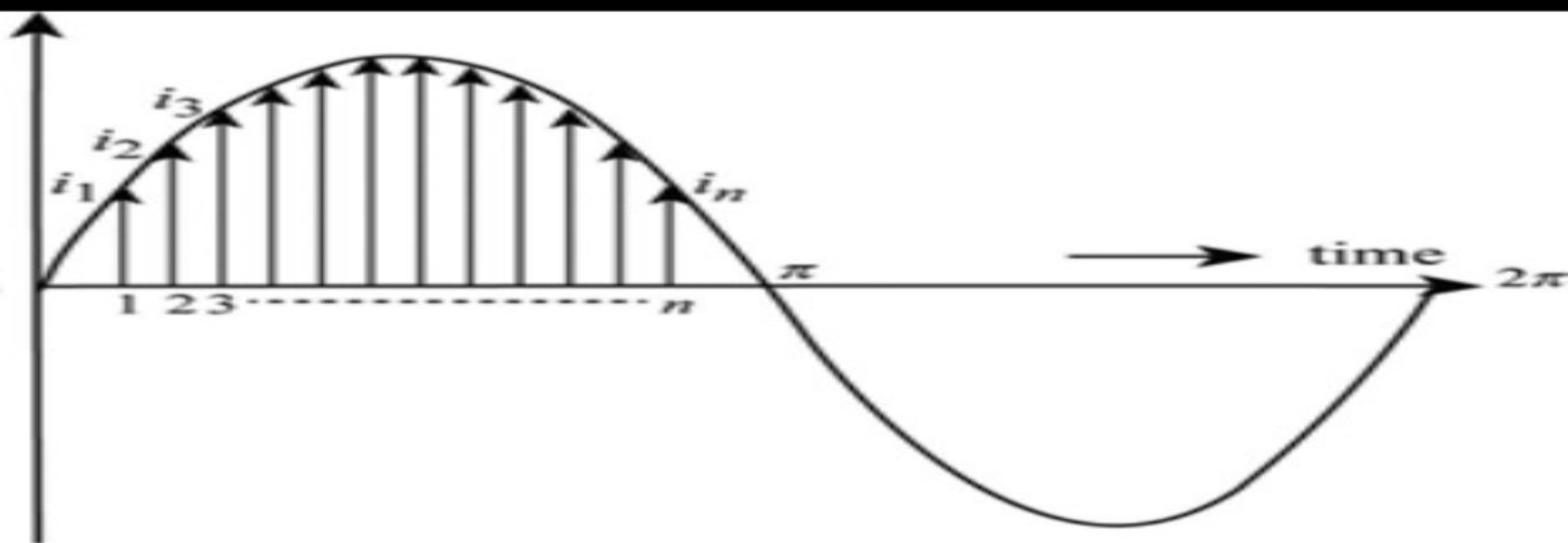


Figure 1

The symbol for A.C is



The simplest a.c voltage V (instantaneous) generated over time by a simple dynamo is represented by the relation

$$V = V \sin \omega t$$

where V is the maximum or peak voltage value, ω is the angular velocity $2\pi f$, t is the oscillating time, ωt is the phase angle and f is the oscillating frequency

PEAK AND R.M.S VALUES OF A.C

The amplitude or peak value of the current I (voltage V) is the maximum numerical value of the current (voltage).

The root mean square (r.m.s.) value of the current $I_{r.m.s}$ (voltage $V_{r.m.s}$)is the effective value of the current (voltage)



The root mean square value is defined as that value of steady current which will produce heat at the same rate in a given conductor.

It occurs when I or V flowing in a.c circuit has phase angle of 45° i.e


$$V_{rms} = V \sin(\omega t) = V \sin 45^\circ$$

$$V_{rms} = V / \sqrt{2} \text{ also}$$

$$I_{rms} = I \sin(\omega t) = I \sin 45^\circ$$


$$I_{rms} = I / \sqrt{2}$$

peaks simultaneous

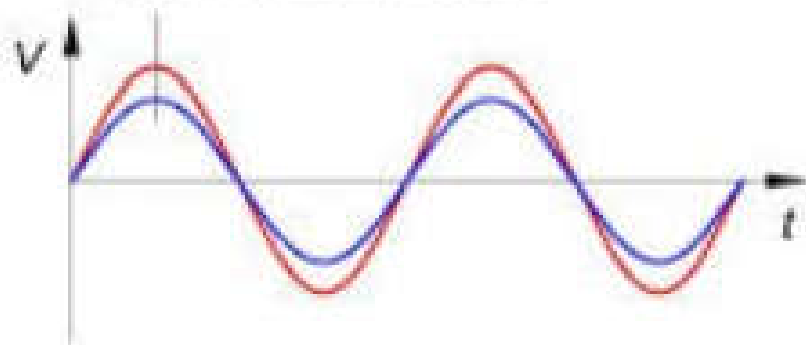

in phase

phase angle $\theta = 90^\circ$

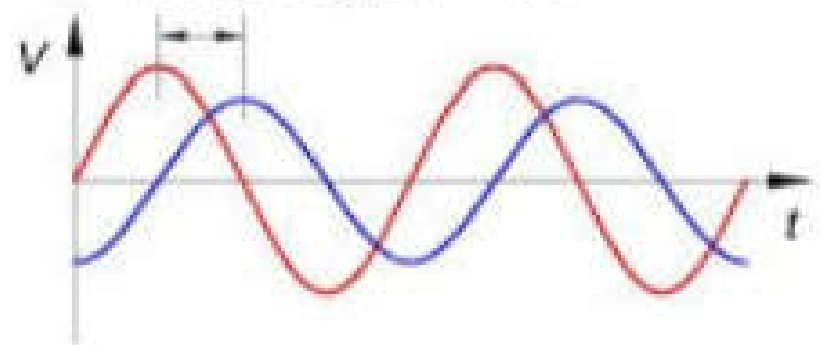


out of phase

In resistance, I and V are in phase.

In capacitor, I leads V by $\pi/2$ while in an inductor, I lags V by $\pi/2$. Hence, from ohm's law, $I = V/R$; $IR = V_{rms}/R$ for the capacitor $I = I \sin \omega t + \pi/2$ and $V = V \sin \omega t$; for the inductor $I = I \sin \omega t - \pi/2$ and $V = V \sin \omega t$

PHASE RELATION IN
A.C

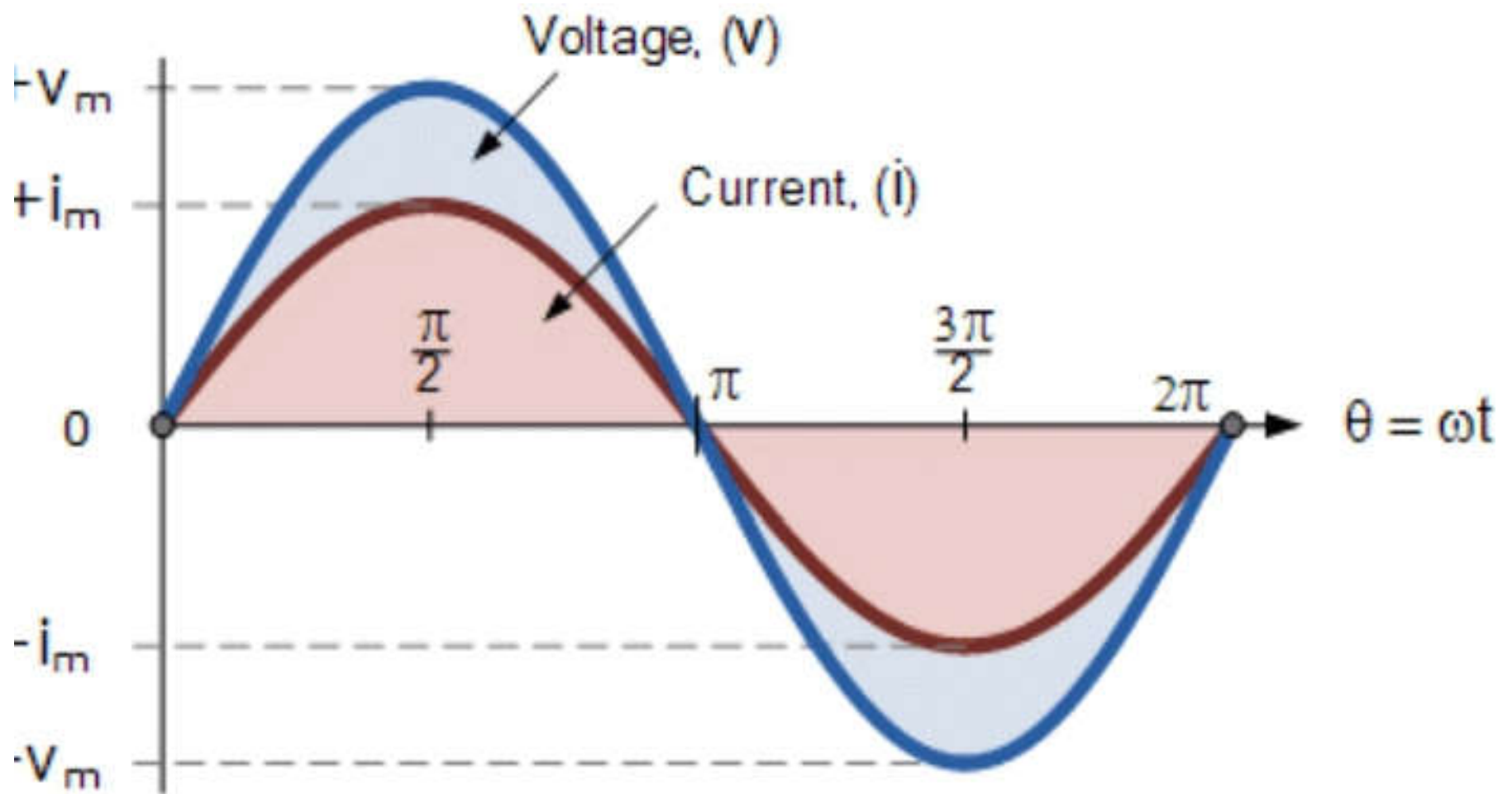

Phase Difference and Phase Shift in an AC Circuit

EXAMPLE

The current I in an a.c circuit is given by the equation $i=30\sin(100\pi t)$ where t is the time in seconds Deduce the following from this equation

- (i) Frequency of the current
- (ii) Peak value of the current
- (iii) rms value of the current

SOLUTION

(i) Frequency of the current: $\omega = 2\pi f = 100\pi$

$$f = 100\pi / 2\pi = 50\text{Hz}$$


(ii) Peak value of the current: $I = 30\text{A}$

(iii) rms value of the current: $I_{\text{rms}} = I / \sqrt{2} = 30 / 1.414 = 21.22\text{A}.$

REACTANCE (X) AND IMPEDANCE(Z)


Reactance is the opposition to the flow of a.c offered by a capacitor or an inductor or both.

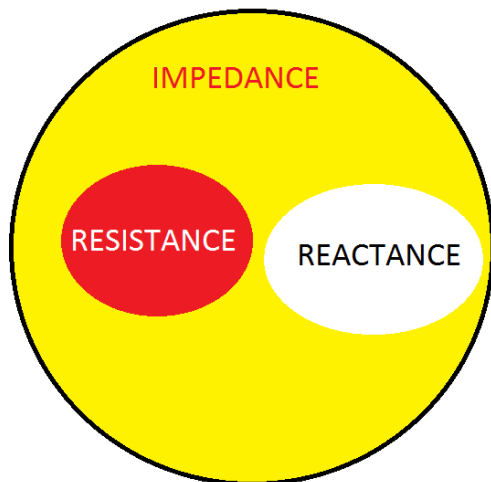Impedance is the overall opposition(effective opposition)of a mixed circuit containing a resistor, an inductor and/ or a capacitor. It is measured in ohms.



Capacitive reactance to an a.c

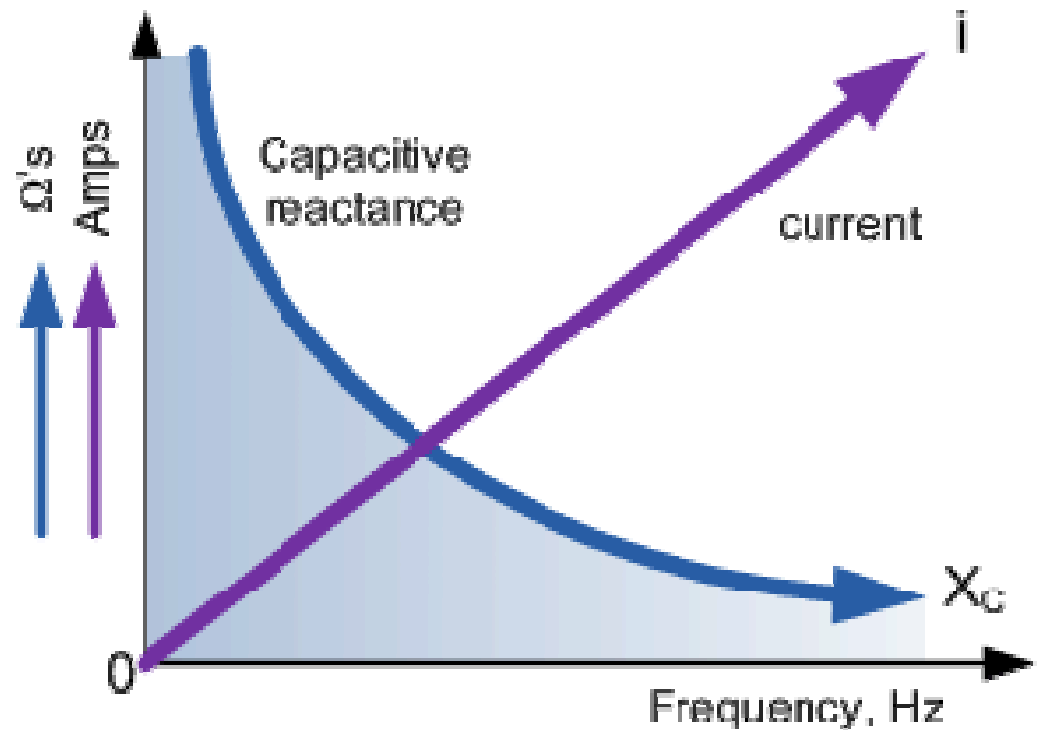The opposition to the flow of current offered by the capacitor is known as capacitive reactance X_c and it is given as $X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$ where C is the capacitance measured in Farads(F).



EXAMPLE


A series RLC circuit comprises a 100ohm resistor, a 3H inductor and a 4μF capacitor. The a.c source of the circuit has an emf of 100V and frequency of $160/\pi$ Hz. Determine the capacitive reactance.

SOLUTION

$$\begin{aligned}X_c &= 1/2\pi fC = 1/2\pi \times 160/\pi \times 4 \times 10^{-6} \\ &= 781.25\text{ohm}\end{aligned}$$

REACTANCE OF AN INDUCTOR

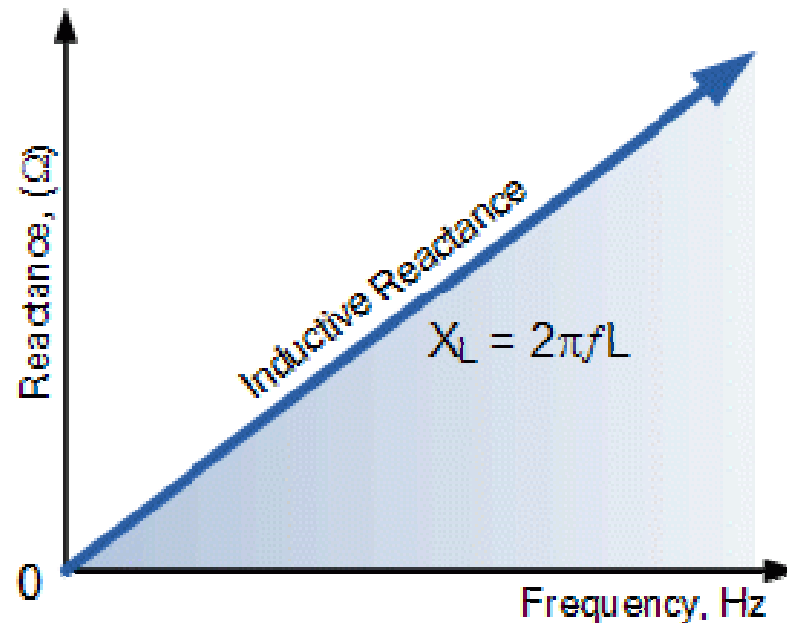X_L is the resistance that is opposing the flow of current in the inductor. It is called inductive reactance and it is given as $X_L = \omega L = 2\pi fL$ where L is the inductance measured in Henry (H)




EXAMPLE

A series RLC circuit comprises a 100ohm resistor, a 3H inductor and a 4μF capacitor. The a.c source of the circuit has an emf of 100V and frequency of $160/\pi$ Hz. Determine the inductive reactance.

Solution

$$X_L = \omega L = 2\pi fL = 2\pi \times 160/\pi \times 3 = 960\text{ohm}$$

VECTOR DIAGRAMS

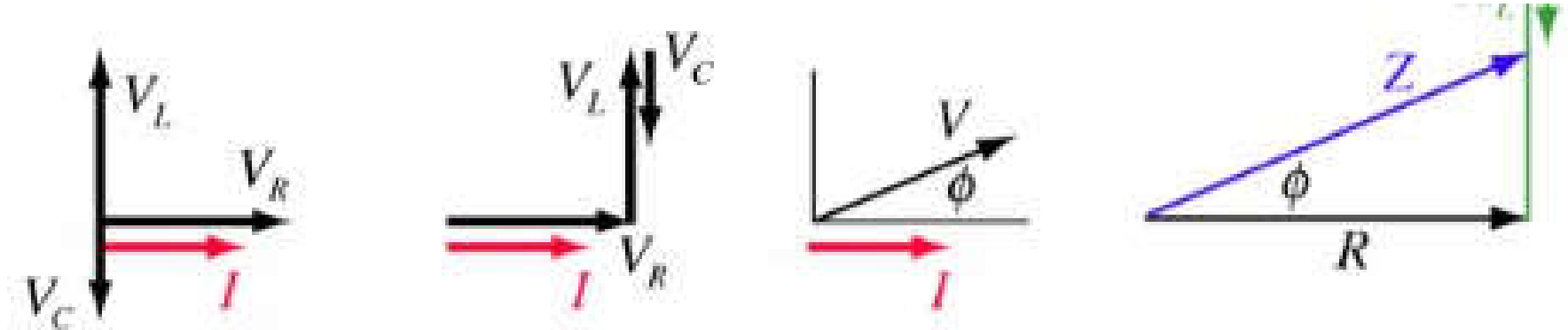

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\phi = \tan^{-1} \frac{V_L - V_C}{V_R}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\phi = \tan^{-1} \frac{X_L - X_C}{R}$$

Phase Relationships in AC Circuits


EXAMPLE

A series RLC circuit comprises a 100ohm resistor, a 3H inductor and a 4μF capacitor. The a.c source of the circuit has an emf of 100V and frequency of $160/\pi$ Hz. Determine the impedance of the circuit.

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{100^2 + (960 - 781.25)^2}$$



$$Z = \sqrt{100^2 + 178.25^2} = 204.82\text{ohm}$$

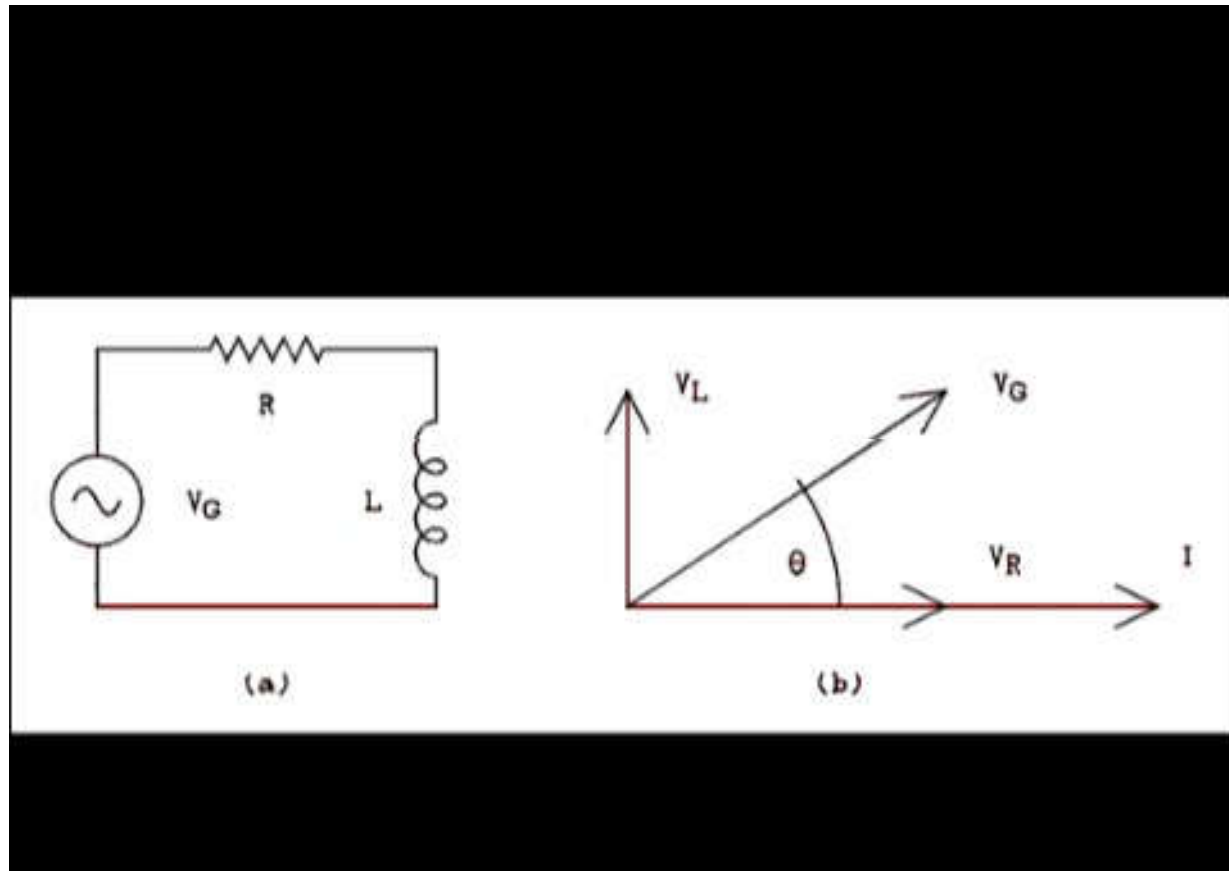IMPEDANCE OF L AND R IN AN L-R SERIES CIRCUIT




Impedance $Z = \sqrt{X_L^2 + R^2}$ while $\tan \theta = X_L / R$

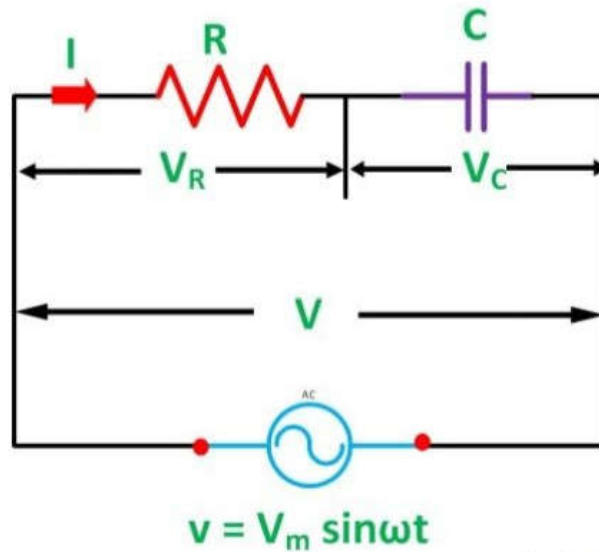 IMPEDANCE OF C AND R IN AN R-C SERIES CIRCUIT



Circuit Globe

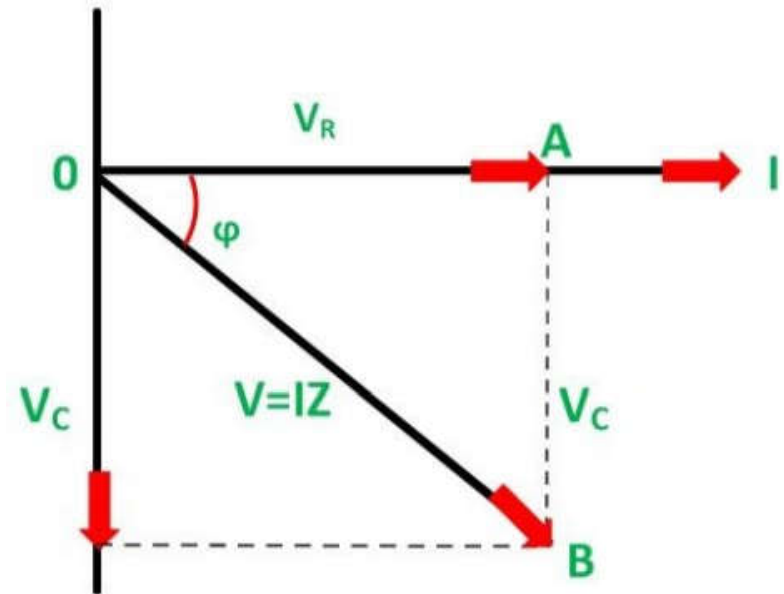


Circuit Globe



Impedance $Z = \sqrt{X_C^2 + R^2}$ while $\tan \phi = X_C/R$


IMPEDANCE OF AN L,R,C SERIES CIRCUIT

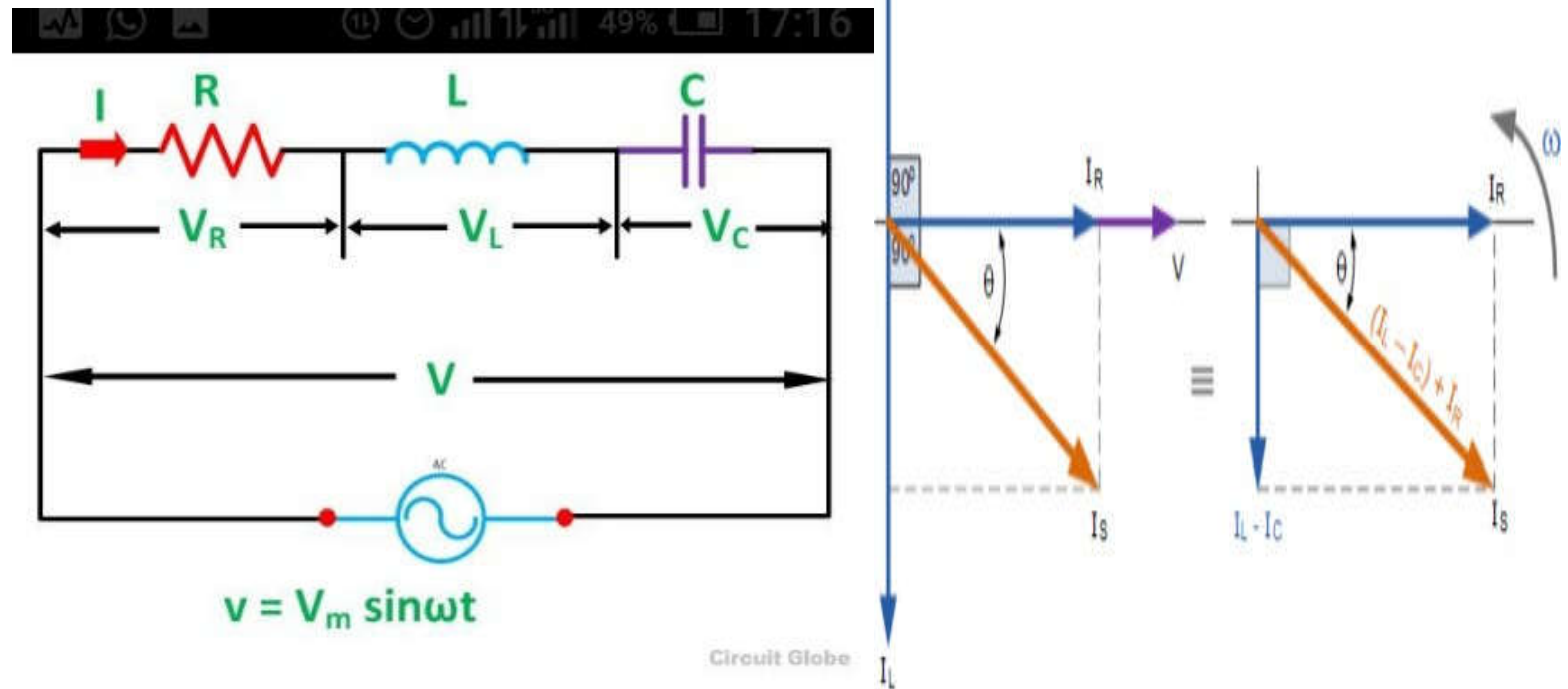

The impedance $Z = \sqrt{R^2 + (X_L - X_C)^2}$
 while $\tan \theta = (X_L - X_C)/R$

POWER IN AN A.C CIRCUIT

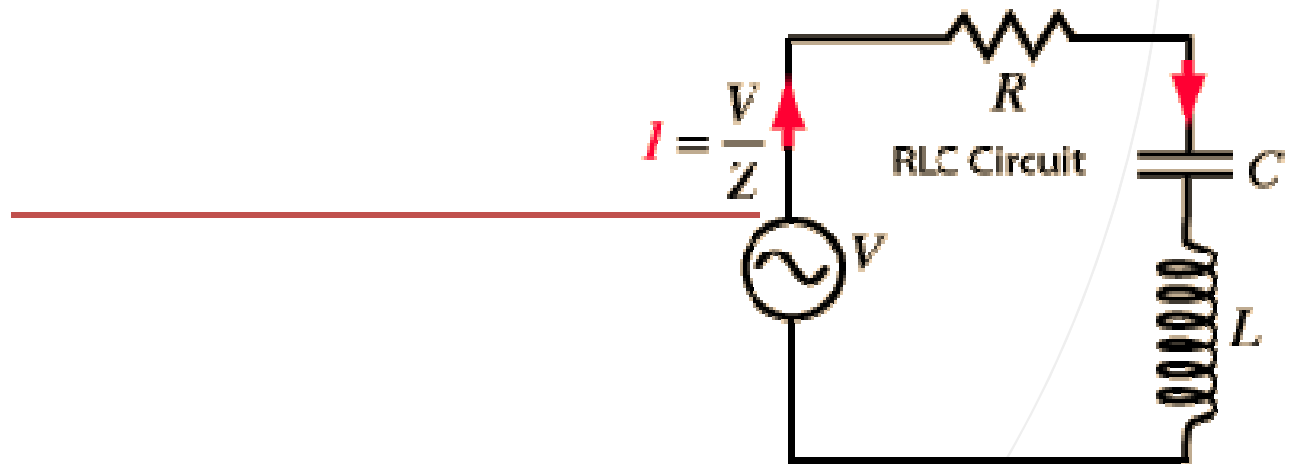The average power in an a.c circuit is given by $P=IV\cos\theta$ where I, V are the rms values of the current and voltage respectively and θ is the angle of lead or lag between them.



The power factor $\cos \theta = R/Z$ (ratio of resistance to impedance). It can have a value between zero and one for θ varying from 90° to 0° .

A power factor of zero means that the device is either a pure reactance, inductance or capacitance.




RESONANCE IN RLC SERIES CIRCUIT

Resonance is said to occur in an a.c series circuit when the maximum current is obtained from such circuit.

From $I = V/Z$, the current I is maximum when impedance Z is minimum. This happens when $X_L = X_C$ i.e $2\pi fL = 1/2\pi fC$.

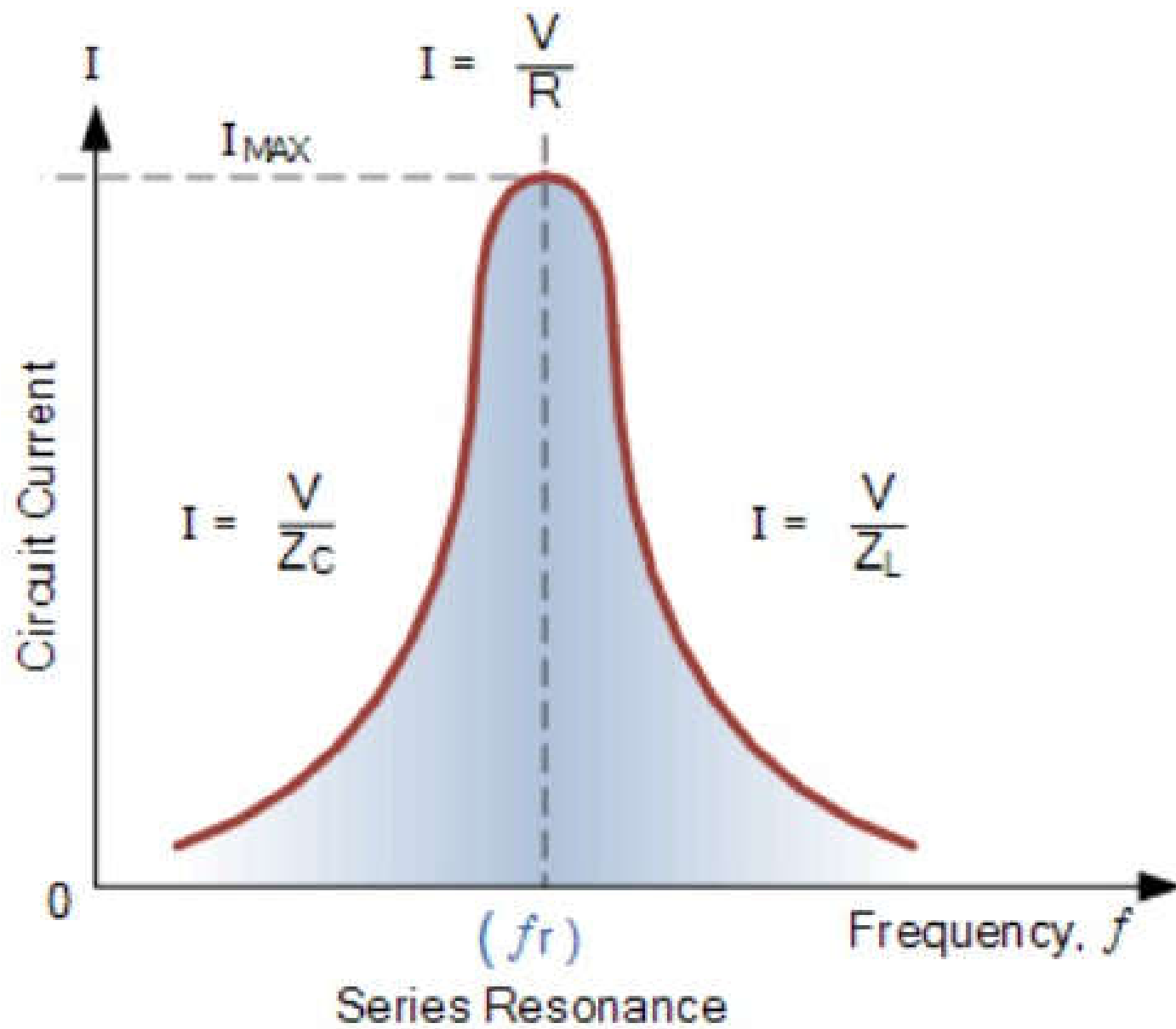The frequency at which this resonance occurs is called resonance frequency f_0 .



To solve for resonance
frequency f_0 :

$$2\pi f_0 L = 1 / 2\pi f_0 c$$

$$f_0 = 1 / 2\pi \sqrt{LC}$$

EXAMPLE

A series RLC circuit comprises a 100ohm resistor, a 3H inductor and a 4 μ F capacitor. The a.c source of the circuit has an emf of 100V and frequency of 160/ π Hz. What is the resonance frequency?

SOLUTION

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi \times \sqrt{3 \times 4 \times 10^{-6}}} = 45.94\text{Hz}$$

TAKE HOME

- (i) The instantaneous current of an a.c power supply is given as $I = 8 \sin(10\pi t)$. Calculate the value of (a) Peak current (b) rms current (c) angular frequency (d) frequency of the instrument.
- (ii) A capacitor of $2.0 \times 10^{-12} \text{F}$ and an inductor are joined in series. What is the value of the inductance that will give the circuit a resonant frequency of 200kHz.
- (iii) What is the value of the angle of lead or lag in alternating current.
- (iv) calculate the peak voltage of a mains supply of 240Vrms.